
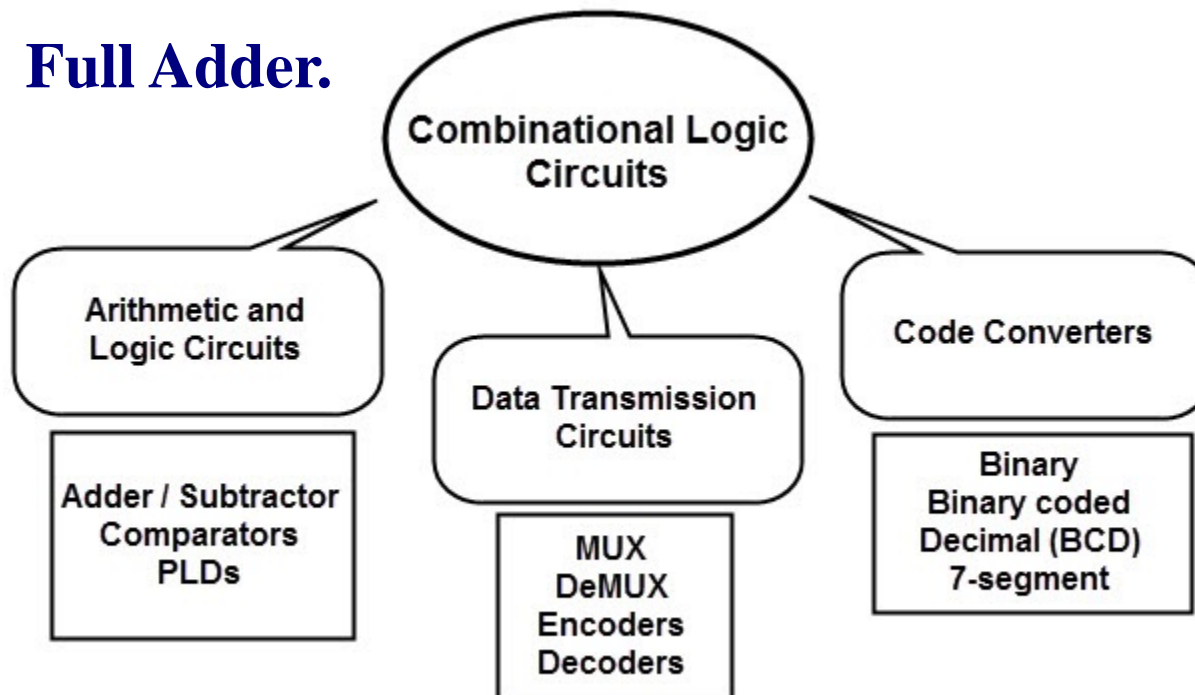


## Digital Engineering


Dr. Hatem Yousry
 
# Agenda

- **Combinational Circuits.**
  - **Binary Adder.**
    - Half Adder.
    - Full Adder.




# Combinational Circuits

 


Block diagram of a combinational circuit

- A combinational logic circuit is a circuit **whose outputs only depend on the current state of its inputs**. In mathematical terms, the each output is a function of the inputs.
- Combinational circuit is a circuit in which we **combine the different gates in the circuit**, for example encoder, decoder, multiplexer and demultiplexer.
- Some of the characteristics of combinational circuits are following –
  - The **output** of combinational circuit at any instant of time, depends only on the levels present at input terminals.
  - The combinational circuit do **not use any memory**. The previous state of input does not have any effect on the present state of the circuit.
  - A combinational circuit can have an **n number of inputs and m number of outputs**

 
 
# Combinational Circuits


- Output is function of input only  
i.e. **no feedback**



When **input** changes, **output** may change (after a delay)
 
# Combinational Circuits


- Combinational circuits are used in a wide variety **applications** including calculators, digital measuring techniques, computers, digital processing, automatic control of machines, industrial processing, digital communications, etc.
- Combinational logic is used in computer circuits **to perform Boolean algebra on input signals and on stored data.** Practical computer circuits normally contain a mixture of combinational and sequential logic.


 
# Combinational Circuits

- **Analysis**

- Given a circuit, find out its *function*
- Function may be expressed as:
  - Boolean function
  - Truth table



- **Design**



- Given a desired function, determine its *circuit*
- Function may be expressed as:
  - Boolean function
  - Truth table



# Reverse Engineering

- Get the Logic Operation.
- Define the inputs and outputs.
- Construct the truth table of the logic function.
- Use K-Map based on Minterm (SOP) to get the logic function.
- Design the Combinational Circuits.



A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

  

A \ B	0	1
0	0	1
1	1	0

  
# Binary Adder

- The binary adder is a combinational circuit that can perform **summation of the input binary numbers**. The most common or basic arithmetic operation is **the addition of binary digits**.
- A combination circuit which performs the additions of **two bits** is called a **half adder** while that performs the addition of **three bits** is a **full adder**.







# Half Adder

 

- The Half adder is the simplest of all adder circuits. **Half adder is a combinational arithmetic circuit that adds two numbers and produces a sum bit (S) and carry bit (C) both as the output.** Let us consider two inputs bits A and B, then sum bit (S) is the **X-OR** of A and B and the carry bit (C) will be the **AND** of A and B. It is evident from the function of a half adder that it requires one **X-OR gate and one AND gate** for its construction. Let us first consider the addition of single bits.

 

 Adds 1-bit plus 1-bit  
Produces Sum and Carry



# Half Adder

- $0 + 0 = 0$
- $0 + 1 = 1$
- $1 + 0 = 1$
- $1 + 1 = 10$

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

for Sum:

A \ B	0	1
0	0	1
1	1	0

(A XOR B)



for Carry:

A \ B	0	1
0	0	0
1	0	1

(A and B)

- Here we perform two operations Sum and Carry, thus we need two **K-maps** one for each to derive the expression.
- Thus, the above equations can be written as

  - $0 + 0 = 00$
- $0 + 1 = 01$
- $1 + 0 = 01$
- $1 + 1 = 10$




- Here the output “1” of “10” becomes the **carry-out**.

# Half Adder

- The “SUM” is the normal output and “CARRY” is the carry-out. Though the half adder is the simplest adder circuit, it has a major disadvantage. **A half adder can add only two input bits (A and B) and is not affected by the carry of the input.**
- As a result, if the input that is given to a half adder has a carry, then it will be neglected and it adds only the bits A and B. But this results in **an incomplete binary addition** and hence it gets its name a half adder. The truth table of half adder is shown in the above table.


Truth Table

Input		Output	
A	B	S	C
0	0	0	0
1	0	1	0
0	1	1	0
1	1	0	1

 

 
# Full Adder

- Full Adder is the adder which adds **three inputs and produces two outputs**. The first two inputs are A and B and the third input is an **input carry as C-IN**.
- The **output carry** is designated as **C-OUT** and the normal output is designated as **S which is SUM**.
- A full adder logic is designed in such a manner that can take eight inputs together to create a byte-wide adder and cascade the carry bit from one adder to the another.



# Full Adder

 


- **Logical Expression for SUM:**
- $= A' B' C-IN + A' B C-IN' + A B' C-IN' + A B C-IN$
- $= C-IN (A' B' + A B) + C-IN' (A' B + A B')$
- $= C-IN \text{ XOR } (A \text{ XOR } B)$
- $= (1,2,4,7)$

- **Logical Expression for C-OUT:**
- $= A' B C-IN + A B' C-IN + A B C-IN' + A B C-IN$
- $= A B + B C-IN + A C-IN$
- $= (3,5,6,7)$

**Full Adder Truth Table:**

Inputs			Outputs	
A	B	C - IN	Sum	C - Out
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

## Full Adder

- Adds 1-bit plus 1-bit plus 1-bit
- Produces **Sum** and **Carry**

	$B'$	$B'$	$B$	$B$
$A'$	$m_0$	$m_1$	$m_3$	$m_2$
$A$	$m_4$	$m_5$	$m_7$	$m_6$
	$C'$	$C$	$C$	$C'$

$C$   $S$

$A$	$B$	$C-IN$	$C$	$S$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

	$B$			
	0	1	0	1
$A$	1	0	1	0
	$C-IN$			

$S = (1, 2, 4, 7)$

$C-IN \text{ XOR } (A \text{ XOR } B)$

	$B$			
	0	0	1	0
$A$	0	1	1	1
	$C-IN$			


$C = (3, 5, 6, 7)$

$A B + B C-IN + A C-IN$

# Implementation of Full Adder


$$S = AB' C\text{-IN}' + A'B C\text{-IN}' + A'B' C\text{-IN} + ABC\text{-IN} = A \oplus B \oplus C\text{-IN}$$

$$C = AB + AC\text{-IN} + BC\text{-IN}$$

 

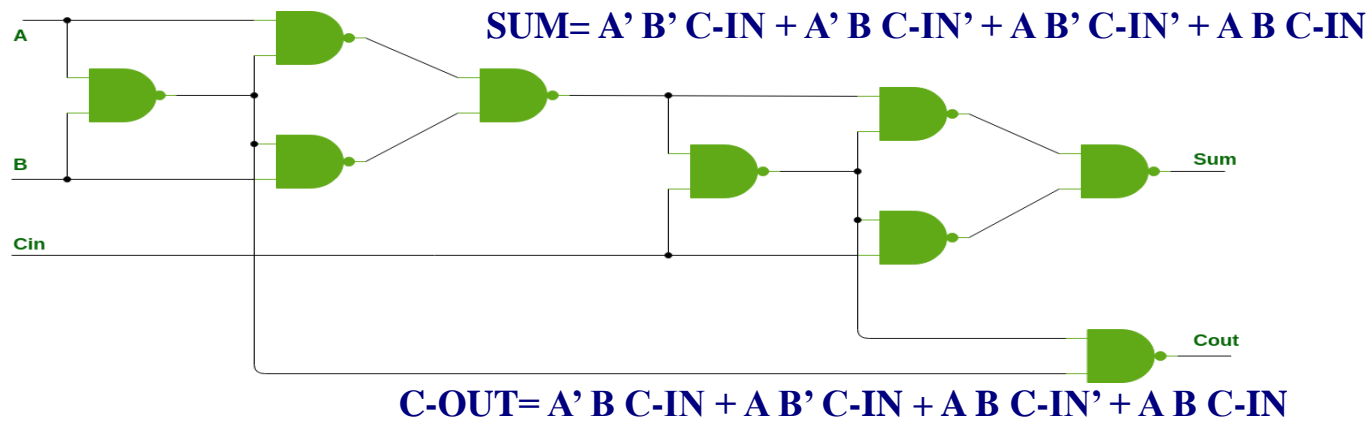
# Implementation of Full Adder

- Implementation of Full Adder using **NAND** gates:



 - Implementation of Full Adder using **NOR** gates:
- Total 9 NOR gates are required to implement a Full Adder.








# Implementation of Full Adder using Half Adders

- **2 Half Adders** and a OR gate is required to implement a Full Adder.
- With this logic circuit, two bits can be added together, **taking a carry from the next lower order of magnitude, and sending a carry to the next higher order of magnitude.**

Inputs			Outputs	
A	B	$C_{IN}$	$C_{OUT}$	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

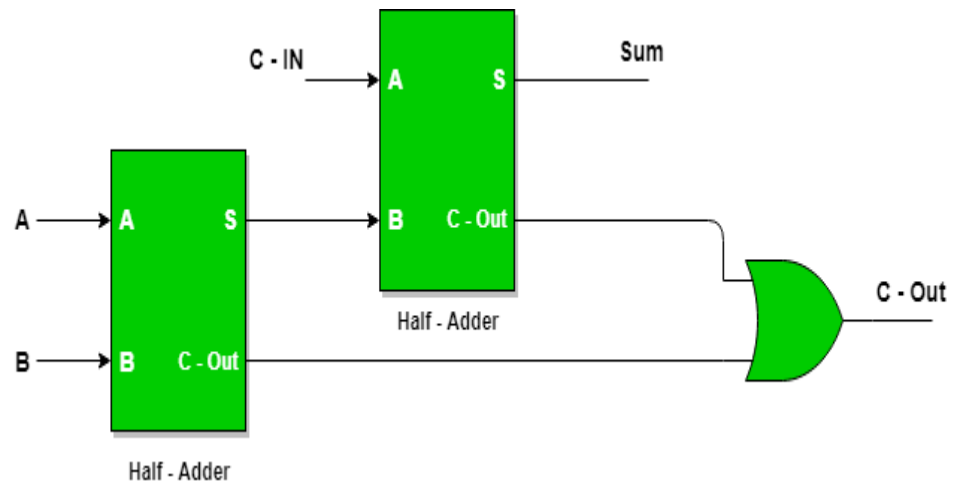

  
# Implementation of Full Adder using Half Adders



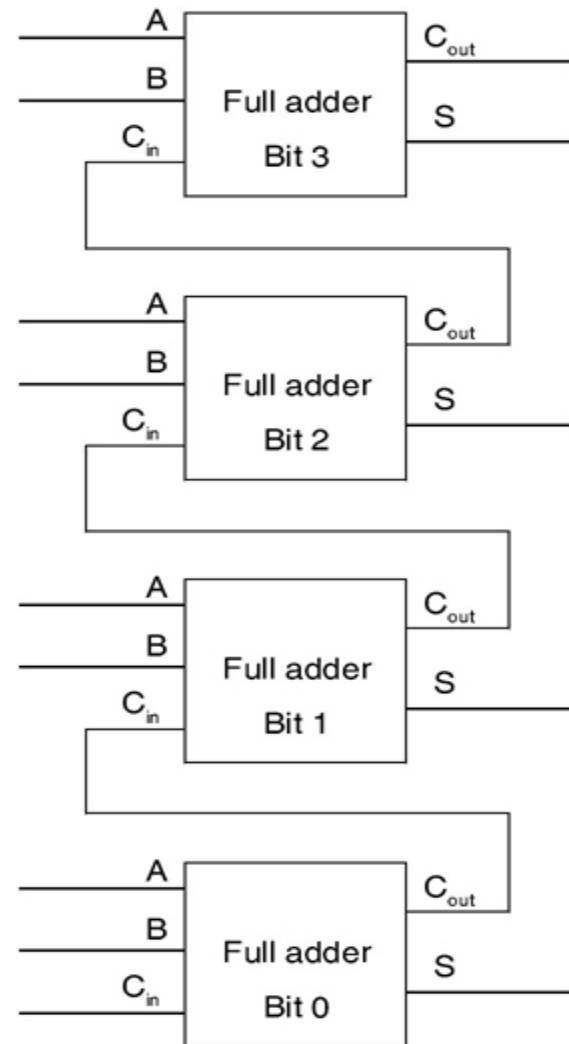
# Multi-bit Adder using Full Adder

- The above-mentioned adder is used to sum up to 2 bits together taking a carry from the next lower order of magnitude and sending a carry to the next higher order of magnitude.
- For a **multi-bit operation**, each bit must be represented by a full adder and all the bits must be **added simultaneously**.
- Thus, to add two 8-bit numbers, we need 8 full adders which can be formed by cascading two of the 4-bit blocks.
- The addition of two 4-bit numbers is shown.




# Binary Adder


 


Carry Propagate Addition
 
$$\begin{array}{r}
 c_3 \ c_2 \ c_1 \\
 + \ x_3 \ x_2 \ x_1 \ x_0 \\
 + \ y_3 \ y_2 \ y_1 \ y_0 \\
 \hline
 Cy \ S_3 \ S_2 \ S_1 \ S_0
 \end{array}$$



# Thank You

  

**Dr. Hatem Yousry**  
**E-mail: [Hyoustry@nctu.edu.eg](mailto:Hyoustry@nctu.edu.eg)**

