
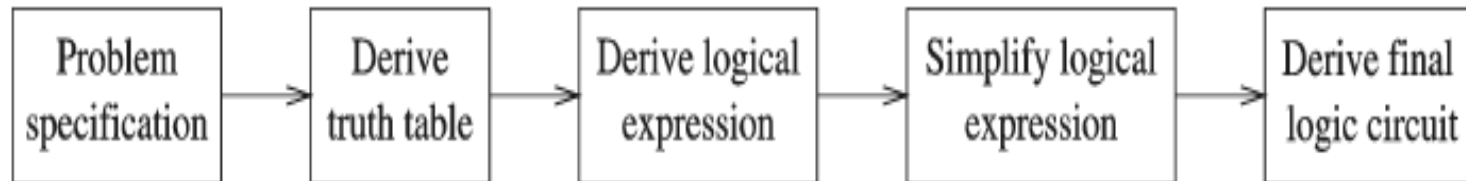


## Digital Engineering

Dr. Hatem Yousry

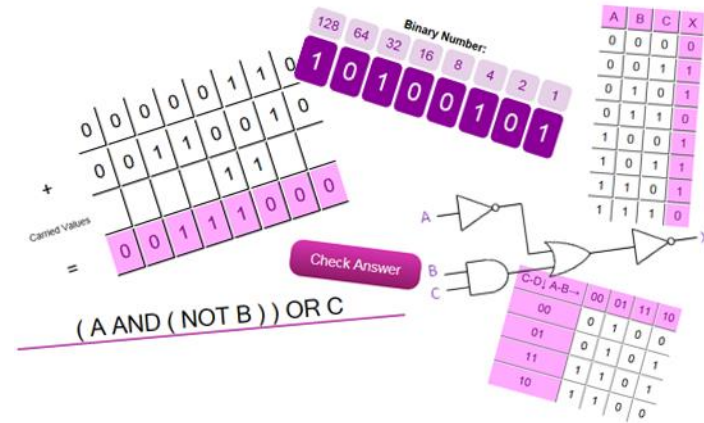
# Agenda

- Conversions.
- Complements.
- Boolean Algebra.



# Digital Engineering (Logic)

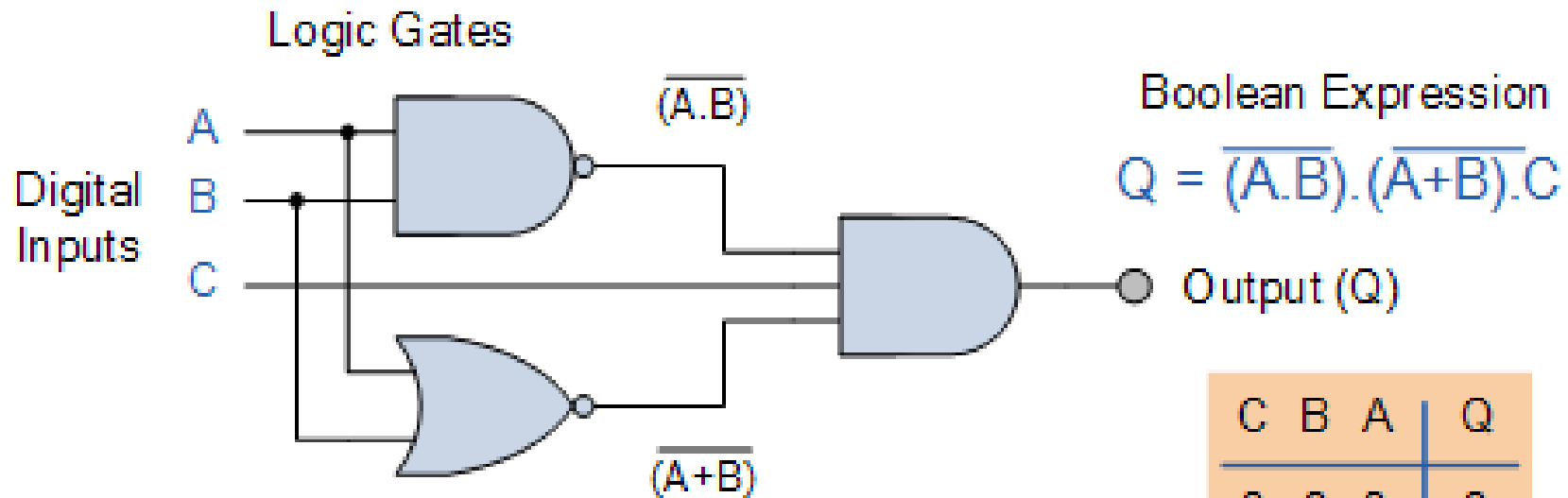1. **Boolean Algebra** – This forms the algebraic expression showing the operation of the logic circuit for each input variable either True or False that results in a logic “1” output.
2. **Truth Table** – A truth table defines the function of a logic gate by providing a concise list that shows all the output states in tabular form for each possible combination of input variable that the gate could encounter.
3. **Logic Diagram** – This is a graphical representation of a logic circuit that shows the wiring and connections of each individual logic gate, represented by a specific graphical symbol, that implements the logic circuit.



Logic Diagram

Typical  
Truth Table

C	B	A	Q
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	0

# Complements

- There are two types of complements for each **base- $r$**  system: the radix (**base**) complement and diminished radix complement.
- Diminished Radix Complement -  $(r-1)$ 's Complement**
  - Given a number  $N$  in base  $r$  having  $n$  digits, the  $(r-1)$ 's complement of  $N$  is defined as:

$$(r^n - 1) - N$$

- Example for 6-digit decimal numbers:**
  - 9's complement is  $(r^n - 1) - N = (10^6 - 1) - N = 999999 - N$
  - 9's complement of 546700 is  $999999 - 546700 = 453299$
- Example for 7-digit binary numbers:**
  - 1's complement is  $(r^n - 1) - N = (2^7 - 1) - N = 1111111 - N$
  - 1's complement of 1011000 is  $1111111 - 1011000 = 0100111$
- Observation:**
  - Subtraction from  $(r^n - 1)$  will never require a borrow
  - Diminished radix complement can be computed digit-by-digit
  - For binary:  $1 - 0 = 1$  and  $1 - 1 = 0$

# Complements

- 1's Complement (*Diminished Radix Complement*)

- All '0's become '1's
- All '1's become '0's

Example  $(10110000)_2$

$\Rightarrow (01001111)_2$

If you add a number and its 1's complement ...

# Binary Logic

- Definition of Binary Logic

- Binary logic consists of binary variables and a set of logical operations.
- The variables are designated by letters of the alphabet, such as  $A, B, C, x, y, z$ , etc, with each variable having two and only two distinct possible values: 1 and 0,
- Three basic logical operations: AND, OR, and NOT.

1. AND: This operation is represented by a dot or by the absence of an operator. For example,  $x \cdot y = z$  or  $xy = z$  is read “ $x$  AND  $y$  is equal to  $z$ ,” The logical operation AND is interpreted to mean that  $z = 1$  if only  $x = 1$  and  $y = 1$ ; otherwise  $z = 0$ . (Remember that  $x, y$ , and  $z$  are binary variables and can be equal either to 1 or 0, and nothing else.)
2. OR: This operation is represented by a plus sign. For example,  $x + y = z$  is read “ $x$  OR  $y$  is equal to  $z$ ,” meaning that  $z = 1$  if  $x = 1$  or  $y = 1$  or if both  $x = 1$  and  $y = 1$ . If both  $x = 0$  and  $y = 0$ , then  $z = 0$ .
3. NOT: This operation is represented by a prime (sometimes by an overbar). For example,  $x' = z$  (or  $\bar{x} = z$ ) is read “not  $x$  is equal to  $z$ ,” meaning that  $z$  is what  $x$  is not. In other words, if  $x = 1$ , then  $z = 0$ , but if  $x = 0$ , then  $z = 1$ , The NOT operation is also referred to as the complement operation, since it changes a 1 to 0 and a 0 to 1.


# Binary Logic

- Truth Tables, Boolean Expressions, and Logic Gates

## AND

$x$	$y$	$z$
0	0	0
0	1	0
1	0	0
1	1	1

$$z = x \cdot y = xy$$

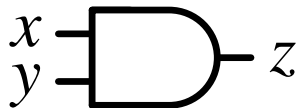

## OR

$x$	$y$	$z$
0	0	0
0	1	1
1	0	1
1	1	1

$$z = x + y$$



## NOT

$x$	$z$
0	1
1	0


$$z = \overline{x} = x'$$








# Switching Circuits

**AND**

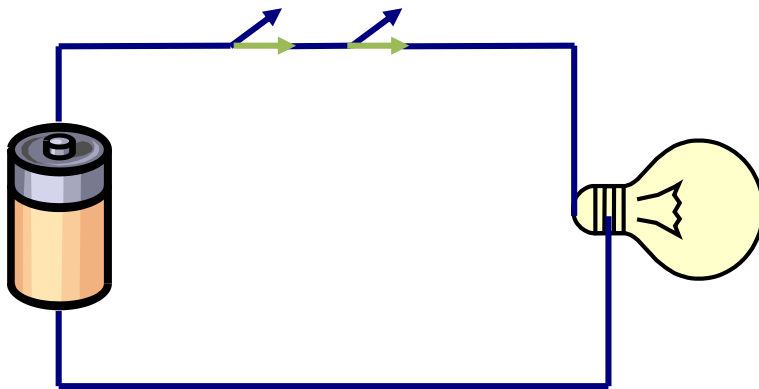


**OR**

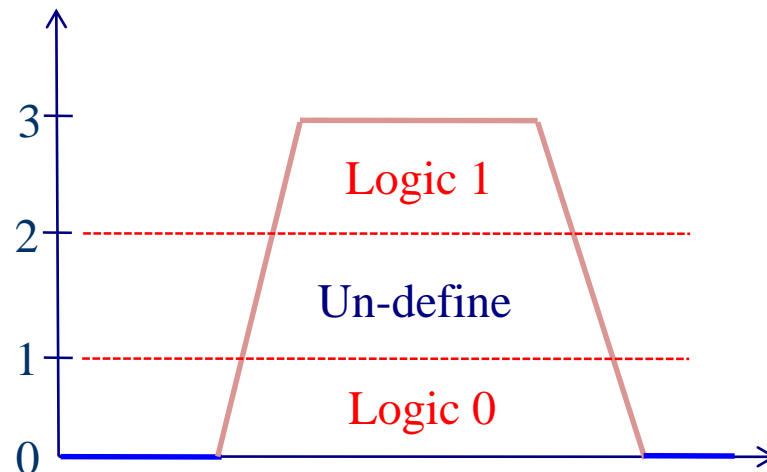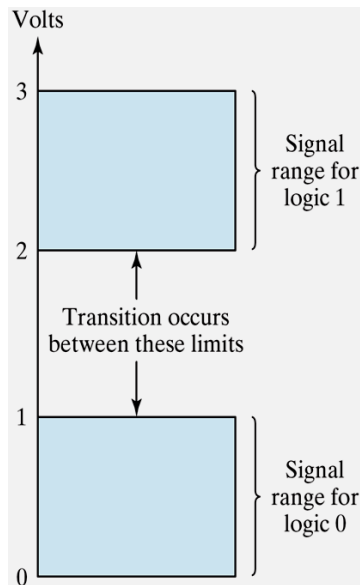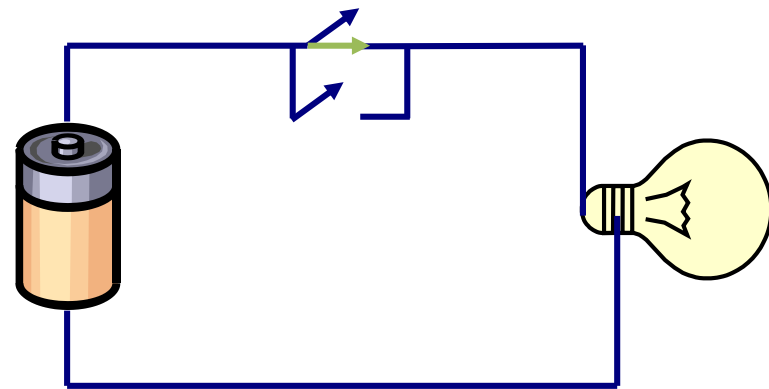

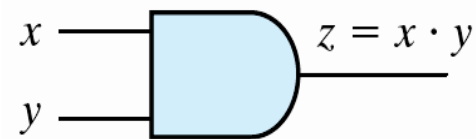
# Binary Logic


- Logic gates
  - Graphic Symbols and Input-Output Signals for Logic gates:




(a) Two-input AND gate

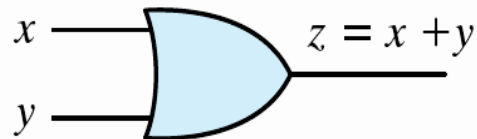

(b) Two-input OR gate

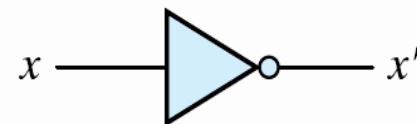


(c) NOT gate or inverter

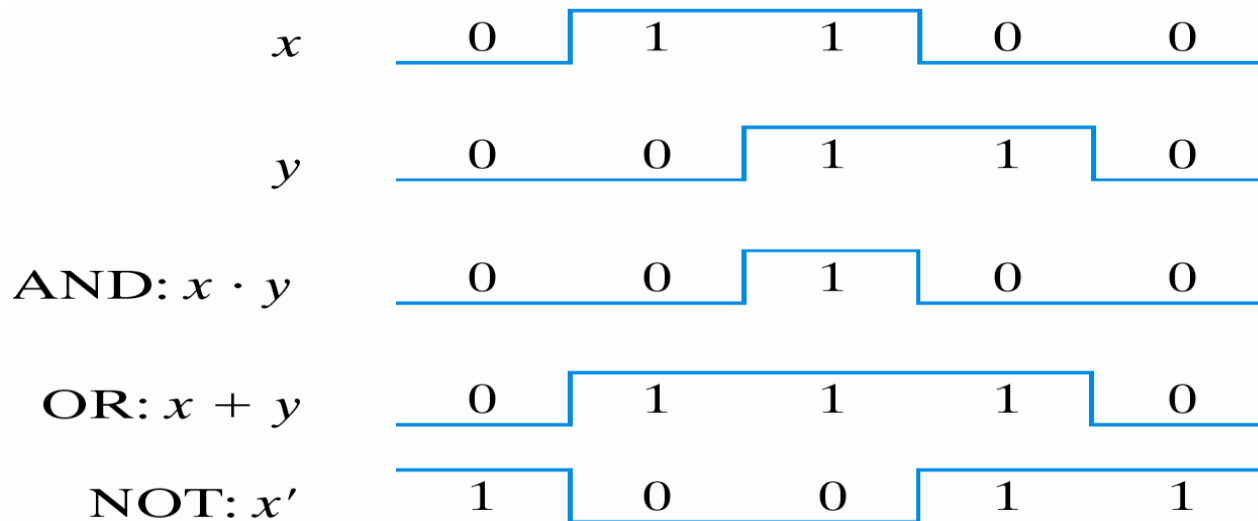

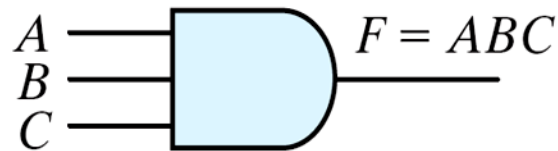
# Binary Logic

- Logic gates
  - Graphic Symbols and Input-Output Signals for Logic gates:




(a) Three-input AND gate

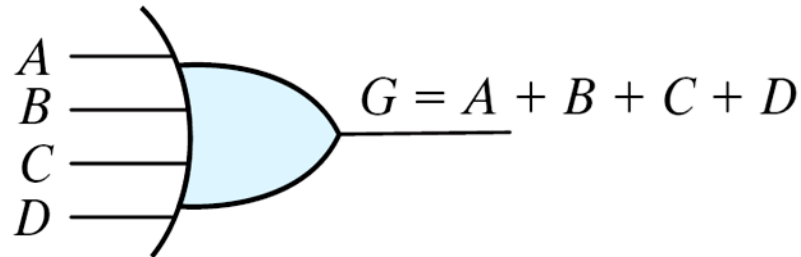


(b) Four-input OR gate

# Logic Chips


5400/7400  
Quad NAND gate

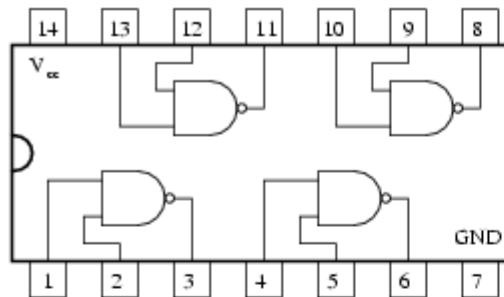


5402/7402  
Quad NOR gate

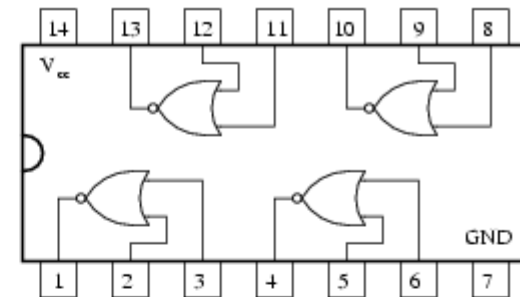


7400 Quad 2-input NAND Gates

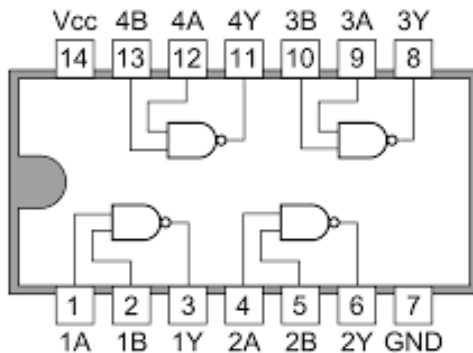


5408/7408  
Quad AND gate

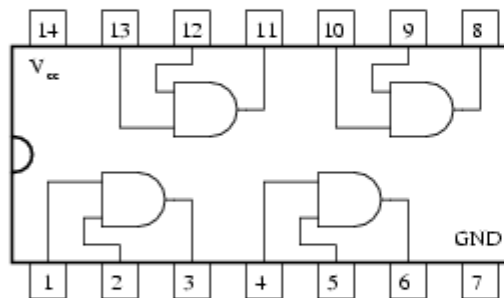


5432/7432  
Quad OR gate

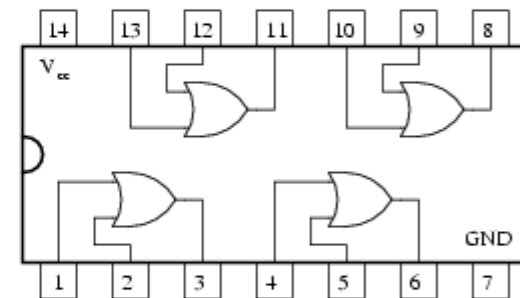

5486/7486  
Quad XOR gate

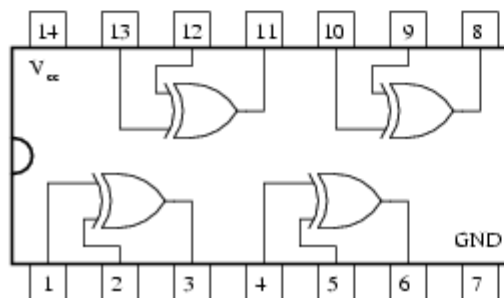

5404/7404  
Hex inverter

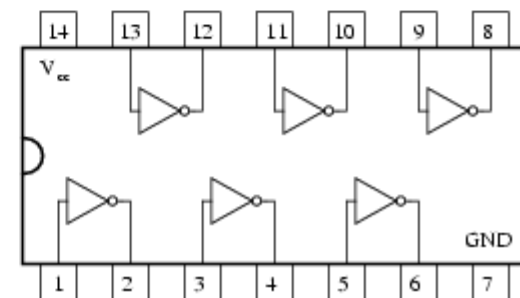

# Integration levels

- SSI (small scale integration)
  - Introduced in late 1960s
  - 1-10 gates (previous examples)
- MSI (medium scale integration)
  - Introduced in late 1960s
  - 10-100 gates
- LSI (large scale integration)
  - Introduced in early 1970s
  - 100-10,000 gates
- VLSI (very large scale integration)
  - Introduced in late 1970s
  - More than 10,000 gates


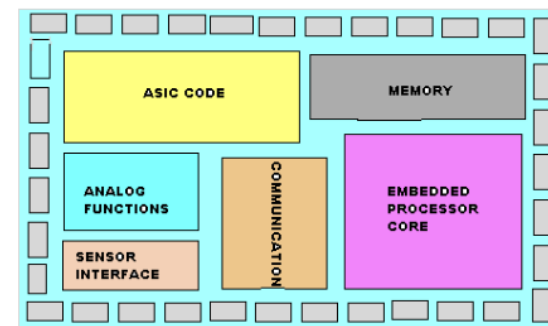
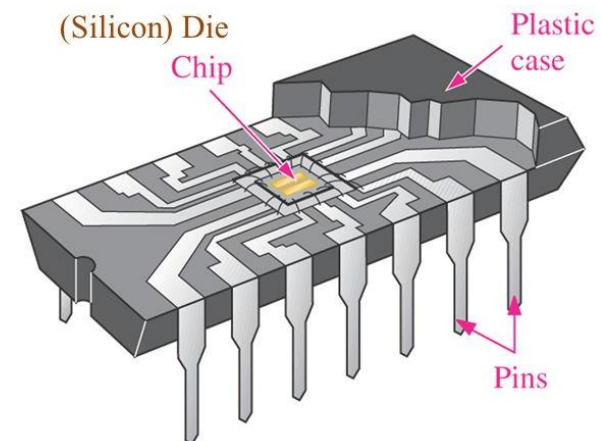


fig 4.1 A SOC DEVICE

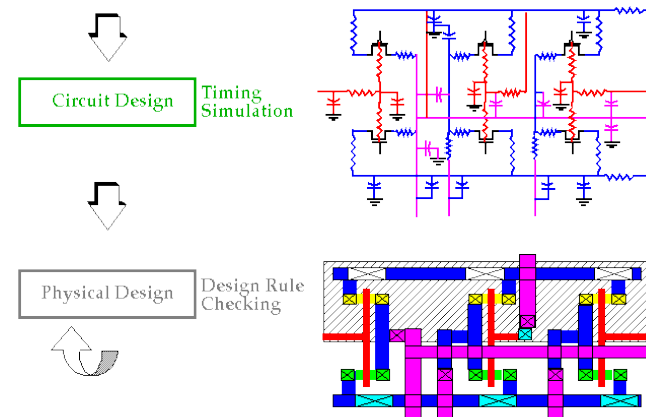


# Logic Functions

- Logical functions can be expressed in several ways:
  - **Truth table**
  - **Logical expressions**
  - **Graphical form**

Truth table:

Input		Output
A	B	$C = (A \cdot B)^I$
0	0	1
0	1	1
1	0	1
1	1	0

Graphical Symbol:

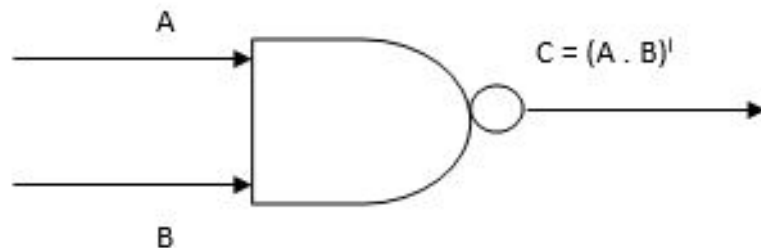

Algebraic Expression is,  $C = (A \cdot B)^I$

# Example: Majority function


- Output is 1 whenever majority of inputs is 1
- We use 3-input majority function

3-input majority function

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1


Logical expression form

$$F = AB + BC + AC$$

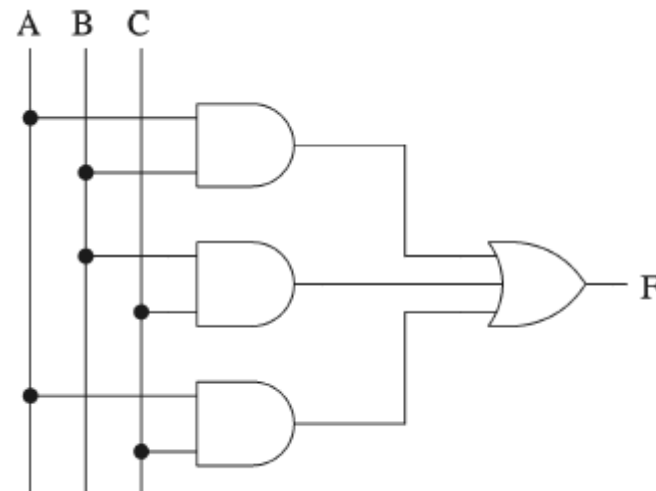
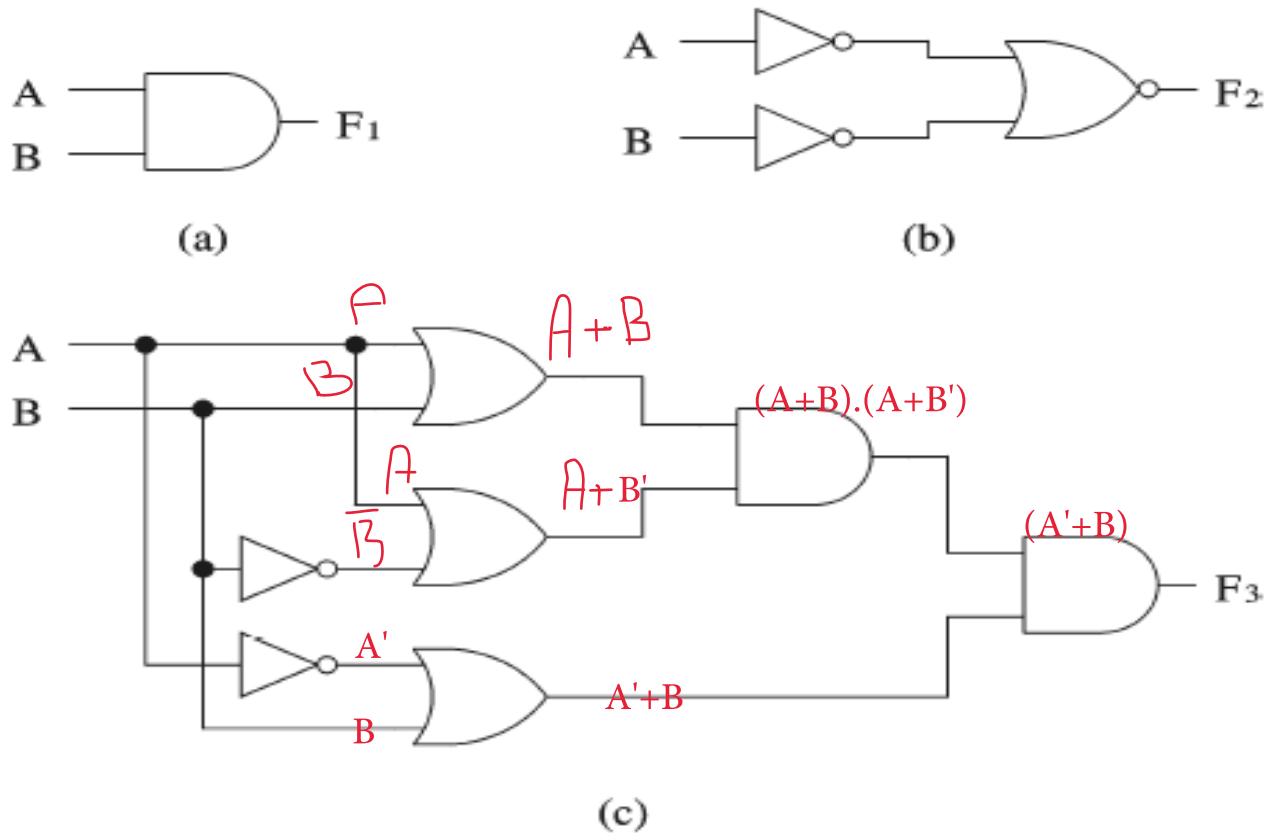
# Logical Equivalence

- All three circuits implement  $F = A \cdot B$  function






# Logical Equivalence

- Proving **logical equivalence** of two circuits
- Derive the logical expression for the output of each circuit
- Show that these two expressions are equivalent, Two ways:
  - You can use the truth table method
    - For every combination of inputs, if both expressions yield the same output, they are equivalent
    - Good for logical expressions with small number of variables
  - You can also use algebraic manipulation
    - Need Boolean identities

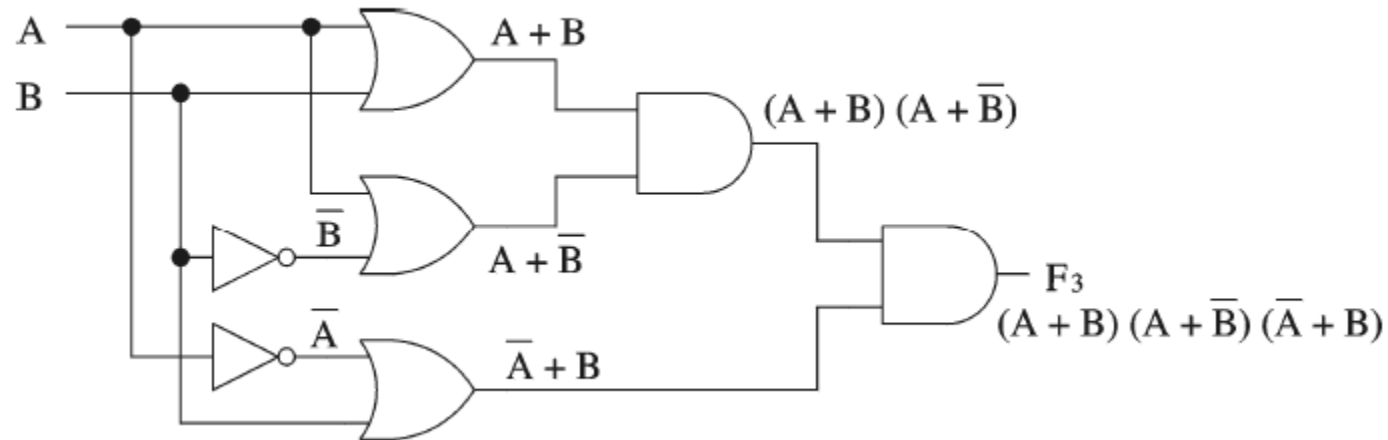
# Derivation of logical expression from a circuit

- Trace from the input to output
- Write down intermediate logical expressions along the path



# Truth Table Method

A	B	F1 = A B	F3 = (A + B) (A + $\bar{B}$ ) ( $\bar{A}$ + B)
0	0	0	0
0	1	0	0
1	0	0	0
1	1	1	1

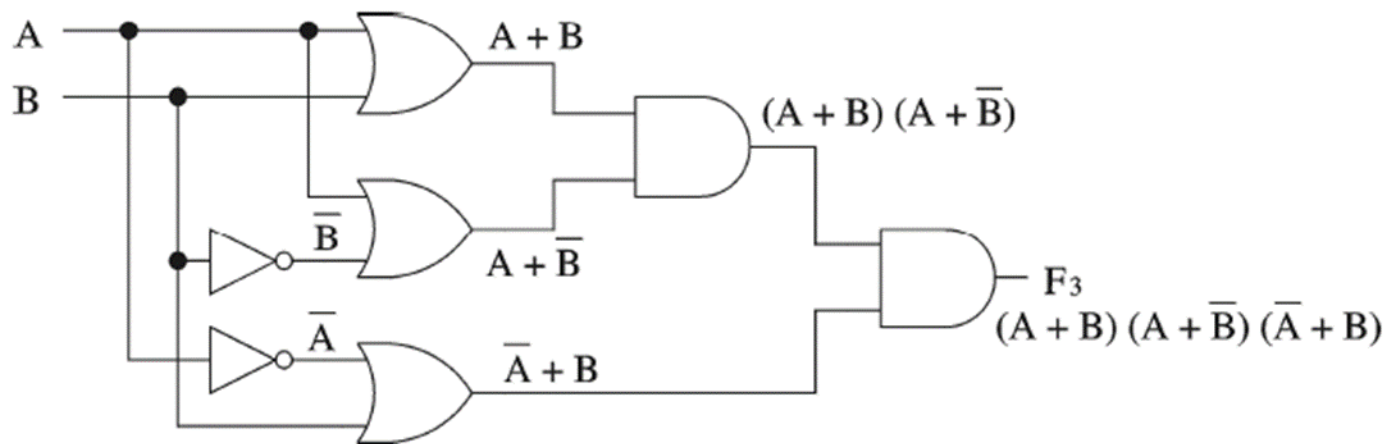

# Boolean Algebra

Name	AND version	OR version
Identity	$x \cdot 1 = x$	$x + 0 = x$
Complement	$x \cdot \overline{x} = 0$	$x + \overline{x} = 1$
Commutative	$x \cdot y = y \cdot x$	$x + y = y + x$
Distribution	$x \cdot (y + z) = xy + xz$	$x + (y \cdot z) = (x + y)(x + z)$
Idempotent	$x \cdot x = x$	$x + x = x$
Null	$x \cdot 0 = 0$	$x + 1 = 1$

# Boolean Algebra

Name	AND version	OR version
Involution	$\overline{\overline{x}} = x$	$---$
Absorption	$x \cdot (x + y) = x$	$x + (x \cdot y) = x$
Associative	$x \cdot (y \cdot z) = (x \cdot y) \cdot z$	$x + (y + z) =$ $(x + y) + z$
de Morgan	$\overline{x \cdot y} = \overline{x} + \overline{y}$	$\overline{x + y} = \overline{x} \cdot \overline{y}$

# Boolean Algebra

- Complement
  - $x+x'=1 \rightarrow 0+0'=0+1=1; 1+1'=1+0=1$
  - $x.x'=0 \rightarrow 0. 0'=0. 1=0; 1. 1'=1. 0=0$
- Duality
  - Form the dual of the expression
  - $a + (bc) = (a + b)(a + c)$
  - Following the replacement rules...
  - $a(b + c) = ab + ac$
- Absorption Property (Covering)
  - $x + xy = x$

$x$	$y$	$xy$	$x+xy$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1


# Basic Theorems

## Postulates and Theorems of Boolean Algebra


Postulate 2	(a) $x + 0 = x$	(b) $x \cdot 1 = x$
Postulate 5	(a) $x + x' = 1$	(b) $x \cdot x' = 0$
Theorem 1	(a) $x + x = x$	(b) $x \cdot x = x$
Theorem 2	(a) $x + 1 = 1$	(b) $x \cdot 0 = 0$
Theorem 3, involution	$(x')' = x$	
Postulate 3, commutative	(a) $x + y = y + x$	(b) $xy = yx$
Theorem 4, associative	(a) $x + (y + z) = (x + y) + z$	(b) $x(yz) = (xy)z$
Postulate 4, distributive	(a) $x(y + z) = xy + xz$	(b) $x + yz = (x + y)(x + z)$
Theorem 5, DeMorgan	(a) $(x + y)' = x'y'$	(b) $(xy)' = x' + y'$
Theorem 6, absorption	(a) $x + xy = x$	(b) $x(x + y) = x$
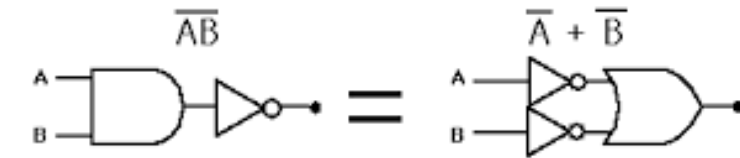
# DeMorgan's Theorem

- $(x + y)' = x'y'$
- $(xy)' = x' + y'$
- By means of truth table



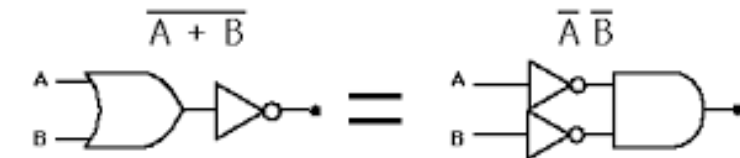A NAND gate is equivalent to an inversion followed by an OR




A NOR gate is equivalent to an inversion followed by an AND


$x$	$y$	$x'$	$y'$	$x+y$	$(x+y)'$	$x'y'$	$xy$	$x'+y'$	$(xy)'$
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0












# De Morgan's Theorem

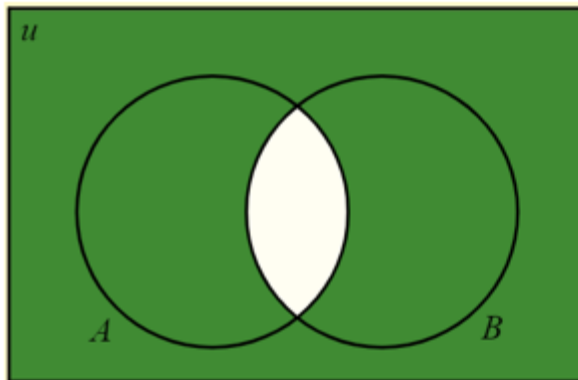

$$(A \cap B)' = A' \cup B'$$

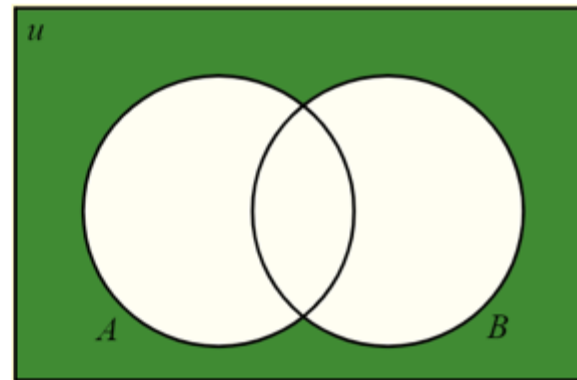

$$(A \cup B)' = A' \cap B'$$

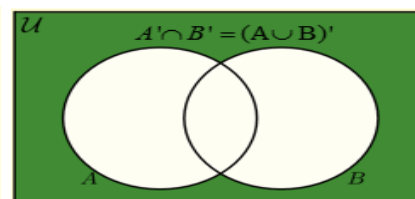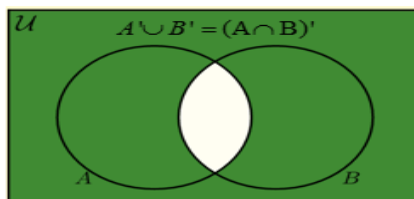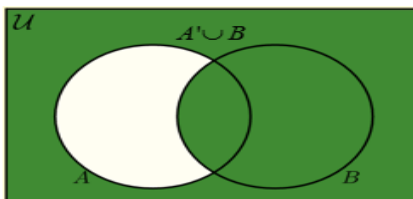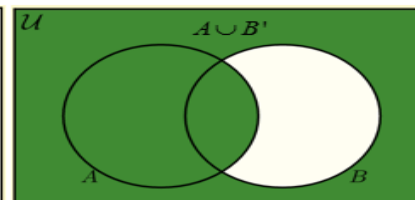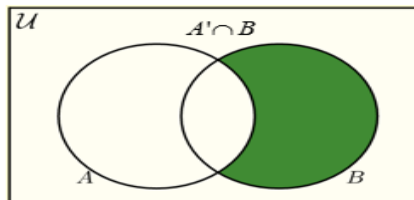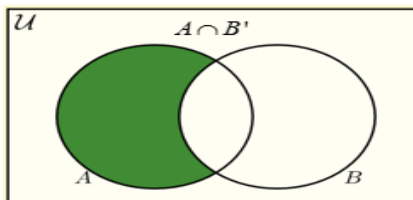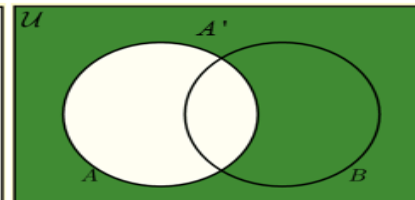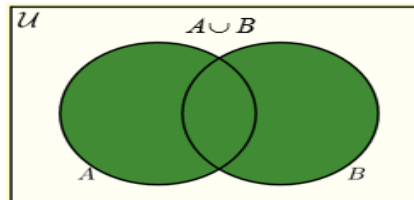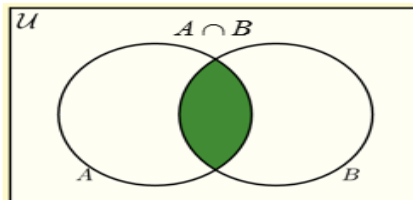

# Consensus Theorem

1.  $xy + x'z + yz = xy + x'z$
2.  $(x+y) \cdot (x'+z) \cdot (y+z) = (x+y) \cdot (x'+z) \text{ -- (dual)}$

$$F = \underbrace{(A + B) \cdot (A' + C)}_{\text{Complemented variable}} \cdot (B + C) \text{ --- Redundancy term}$$

# Operator Precedence

- The operator precedence for evaluating Boolean Expression is

- **Parentheses**
- **NOT**
- **AND**
- **OR**

Highest




Lowest

( ) [ ]  
 ! ++ --  
 \* / % ^  
 + -  
 < <= > >=  
 == !=  
 &&  
 ||  
 ? :  
 = += -= \*= /=

# Logic Circuit Design Process

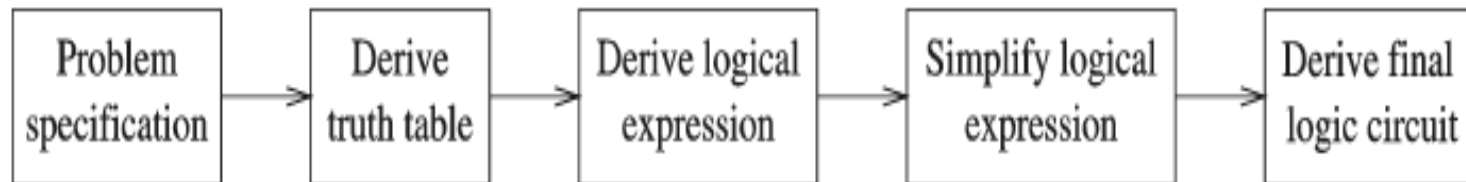
- Problem specification.
- Truth table derivation.
- Derivation of logical expression.
- Simplification of logical expression.
- Implementation.




	Inputs				Output		
	A	B	C	D			
0	0	0	0	0			
1	0	0	0	1			
2	0	0	1	0			
3	0	0	1	1			
4	0	1	0	0			
5	0	1	0	1			
6	0	1	1	0			
7	0	1	1	1			
8	1	0	0	0			
9	1	0	0	1			
10	1	0	1	0			
11	1	0	1	1			
12	1	1	0	0			
13	1	1	0	1			
14	1	1	1	0			
15	1	1	1	1			

X =

### Logic Diagram

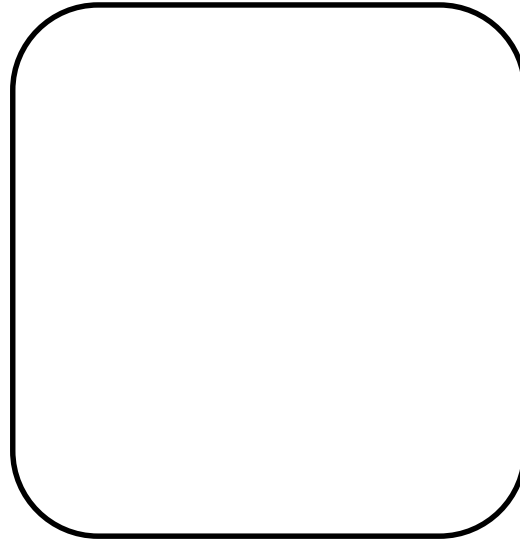

X =

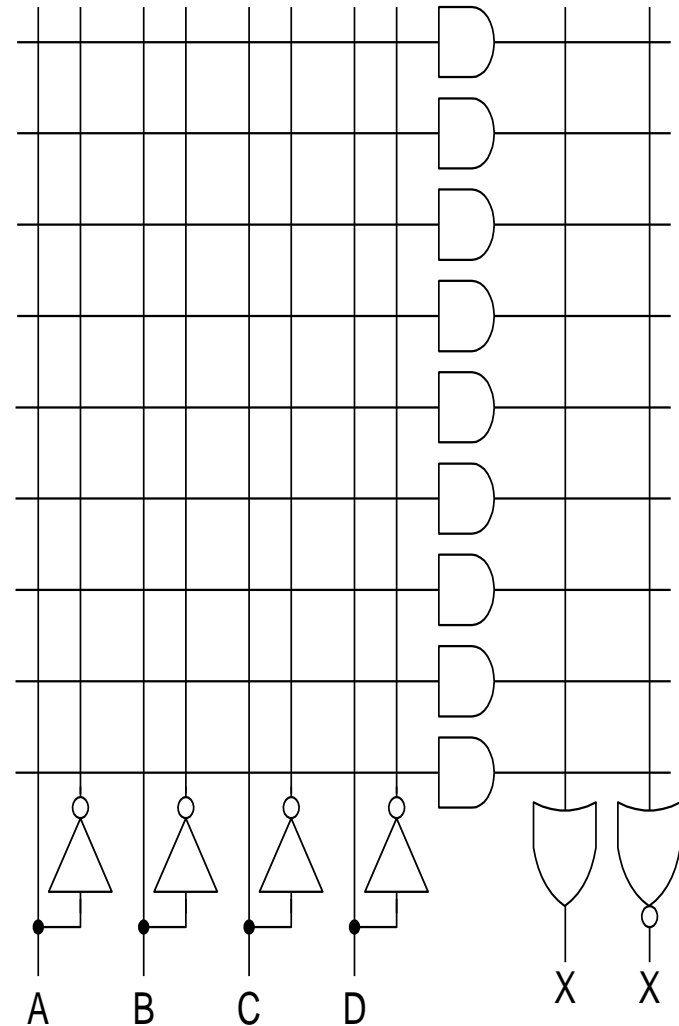


# Examples

- $F_1 = x y z'$
- $F_2 = x + y'z$
- $F_3 = x' y' z + x' y z + x y'$
- $F_4 = x y' + x' z$

$x$	$y$	$z$	$F_1$	$F_2$	$F_3$	$F_4$
0	0	0	0	0	0	0
0	0	1	0	1	1	1
0	1	0	0	0	0	0
0	1	1	0	0	1	1
1	0	0	0	1	1	1
1	0	1	0	1	1	1
1	1	0	1	1	0	0
1	1	1	0	1	0	0

# Boolean Functions


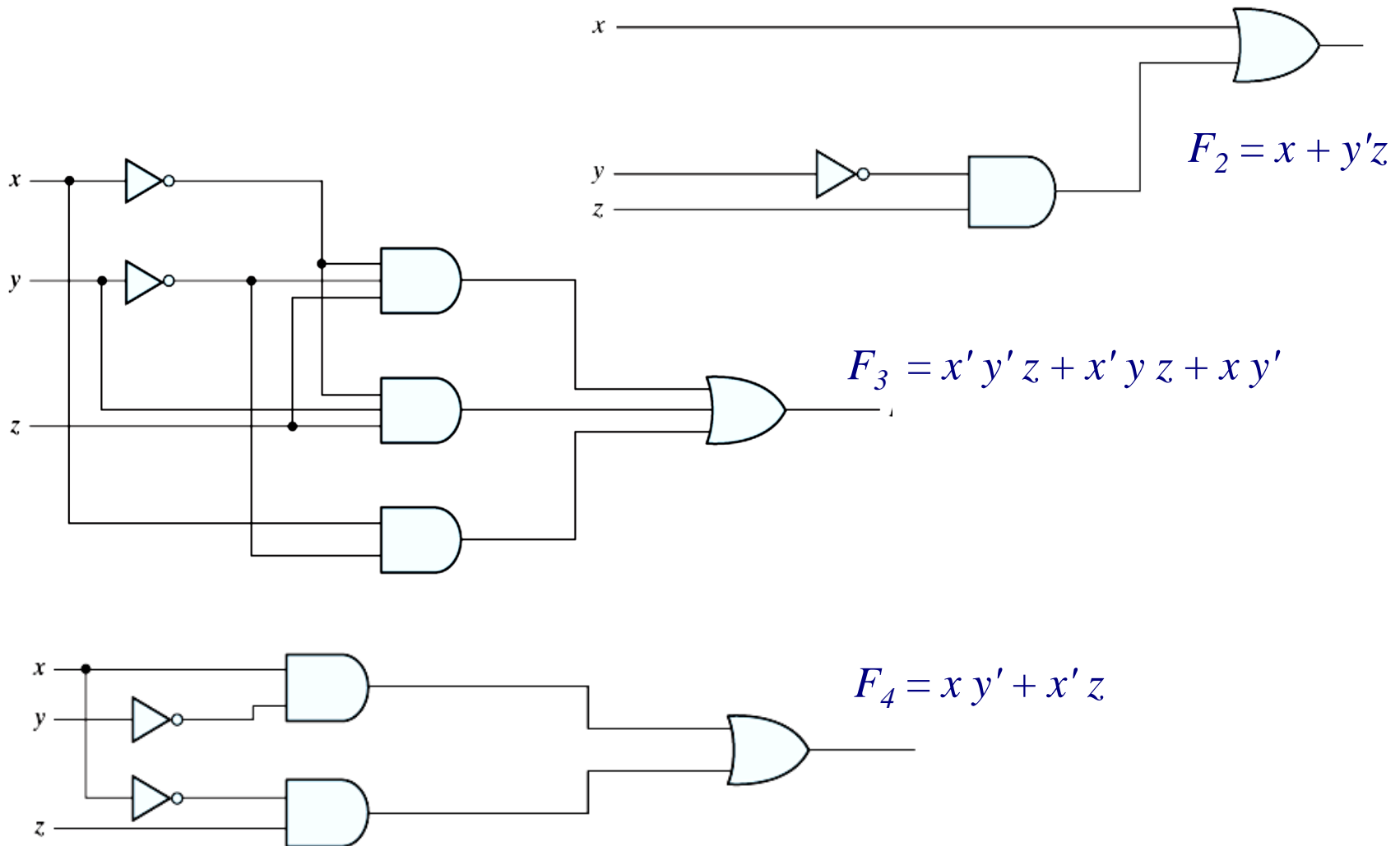


# Example

1.  $x(x'+y) = xx' + xy = 0 + xy = xy$
2.  $x+x'y = (x+x')(x+y) = 1(x+y) = x+y$
3.  $(x+y)(x+y') = x+xy+xy'+yy' = x(1+y+y') = x$
4.  $xy + x'z + yz = xy + x'z + yz(x+x') = xy + x'z + yzx + yzx' = xy(1+z) + x'z(1+y) = xy + x'z$
5.  $(x+y)(x'+z)(y+z) = (x+y)(x'+z)$ , by duality from function 4. (*consensus theorem* with duality)



# Thank You

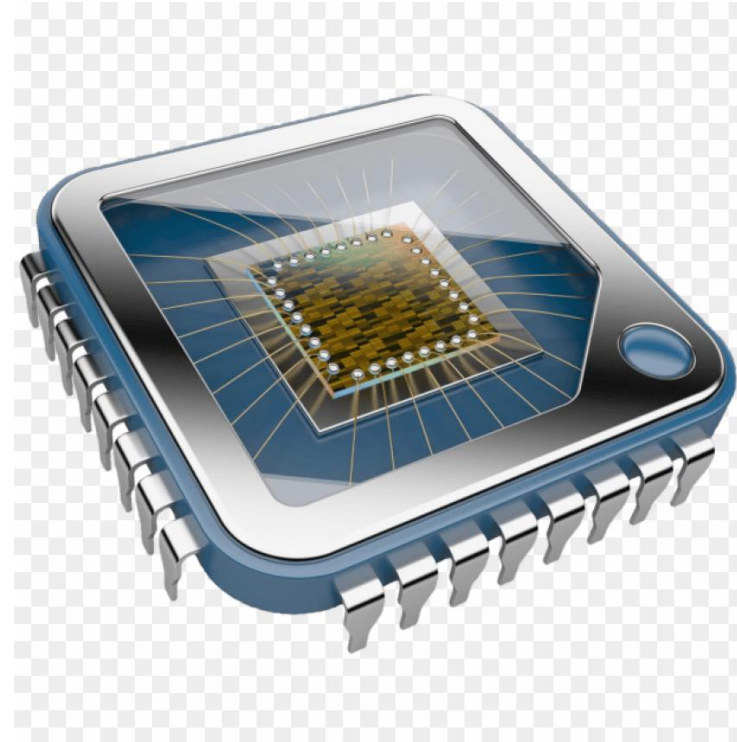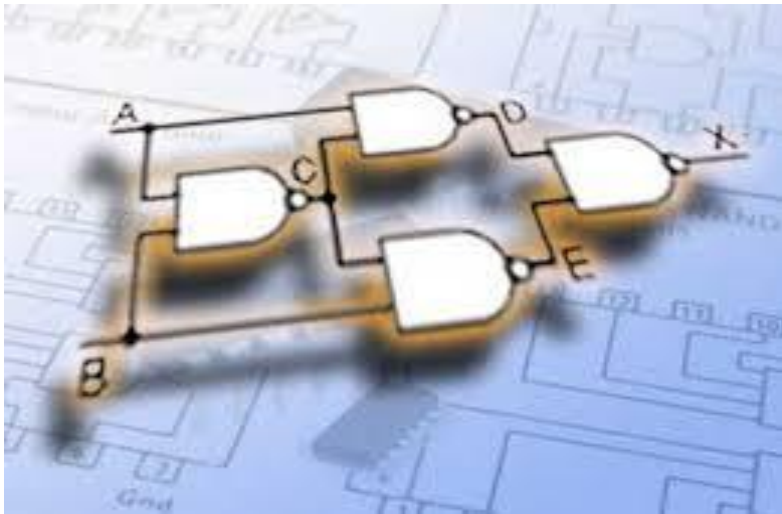

**Dr. Hatem Yousry**  
**E-mail: [Hyoustry@nctu.edu.tw](mailto:Hyoustry@nctu.edu.tw)**

