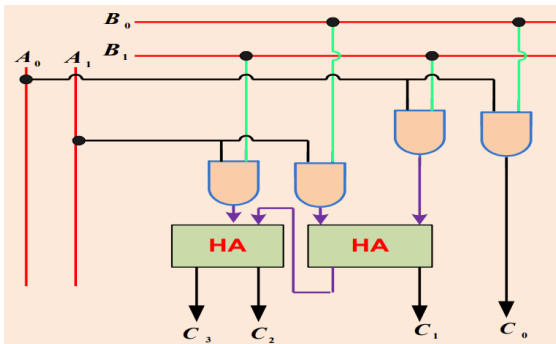


Task1:

1- Identify the main components of the given combinational logic system and extract the relations between each block.




❖ Main Components:

- AND gates
- Partial Product

HALF ADDER:

XOR

AND GATE

 

❖ Main Components:

- AND gate
- OR gate
- XOR gate

Relations

$A_0 B_0 + 0 \rightarrow P_0$

$B_0 A_1 + B_1 A_0 \rightarrow P_1$, and C_1 carryout in case that $B_0 A_1 = 1$ and $B_1 A_0 = 1$

$C_1 + B_1 A_1 \rightarrow P_2$, and C_2 carryout in case that $C_1 = 1$ and $B_1 A_1 = 1$

$C_2 \rightarrow P_3$

Define the different types of logic components in the given combinational logic system.

Input:

❖ **Switches**

- A0 - A1 - B0 - B1

❖ **System**

- **AND Gate**

Outputs 1 only if ALL inputs are 1. Think of it as a two-key lock requiring both keys to turn for the door to open.

Otherwise, it outputs 0. Even one missing key (0) keeps the door shut.

- **HALF ADDER**

It's a basic digital circuit that performs the addition of two single binary digits (bits). In this case the first half adder used to add (A0 B1 + A1B0), the sum is C1 and the carryout will be used as input to the second half adder which is adding (C1 + A1B1)

XOR gate

Outputs 1 if only ONE input is 1. Imagine an exclusive club door: you can only enter if either key (1) is used, not both.

Outputs 0 if BOTH inputs are the same (0 or 1). Both keys being the same (both 0s or both 1s) gets you denied entry.

AND Gate

❖ **Outputs**

- C0

- C1

- C2

- C3

3. Explain the operation of the given combinational logic system as shown in Figure1 , make a good use of Truth Tables and Karnaugh Map (K-Map).

A1	A0	B1	B0	P3	P2	P1	P0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0
0	1	0	1	0	0	0	1
0	1	1	0	0	0	1	0
0	1	1	1	0	0	1	1
1	0	0	0	0	0	0	0
1	0	0	1	0	0	1	0
1	0	1	0	0	1	0	0
1	0	1	1	0	1	1	0
1	1	0	0	0	0	0	0
1	1	0	1	0	0	1	1
1	1	1	0	0	1	1	0
1	1	1	1	1	0	0	1

P0

	00	01	11	10
00	0	0	0	0
01	0	1	1	0
11	0	1	1	0
10	0	0	0	0

P1

	00	01	11	10
00	0	0	0	0
01	0	0	1	1
11	0	1	0	1
10	0	1	1	0



P2

	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	1
10	0	0	1	1

P3

	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	1	0
10	0	0	0	0

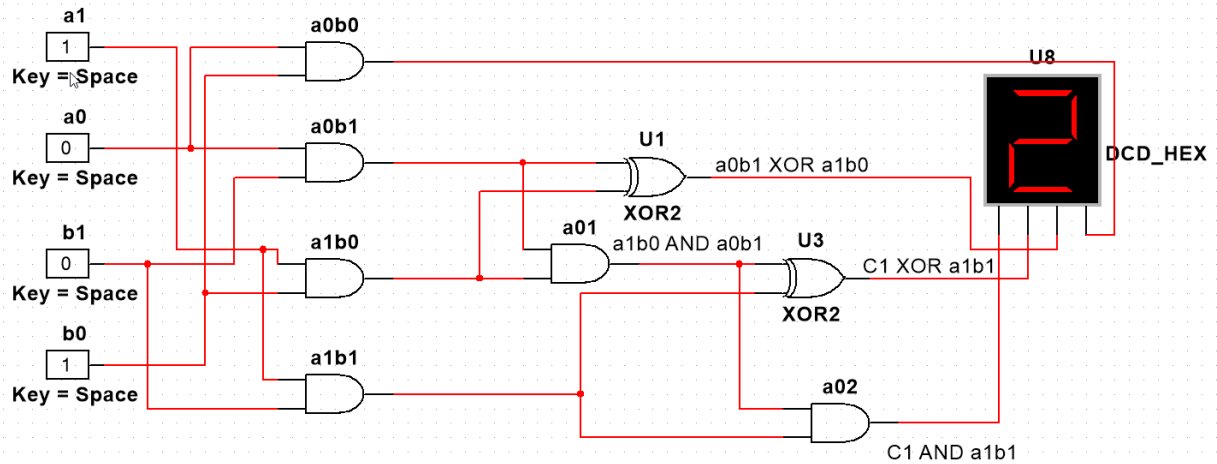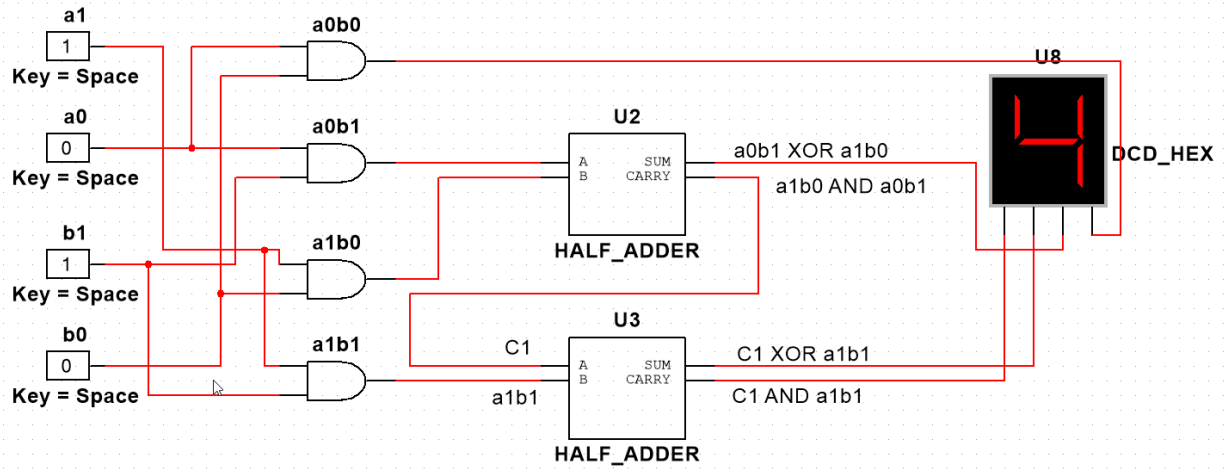4. Explain and Sketch the logic gates diagram of the 2-bits binary multiplier for Structural Design. and compare it with the Behaviour Design.



5. Analyze the main differences between Structural Design and Behavior Design for 2-bits binary multiplier as shown in Figure 2.

Structural Design:

Focus: Building the multiplier by directly implementing its internal hardware structure.

Complexity: Can be more complex for larger multipliers, requiring detailed understanding of gate-level logic and careful manual wiring.

Method: This involves manually defining the logic gates and their connections. You directly specify how each gate operates on the input bits to generate the partial products and final product.


Behavioral Design:

Focus: Describing the desired behavior of the multiplier without explicitly defining its hardware structure.

Complexity: Simpler to design, especially for large multipliers, as you focus on the algorithm rather than intricate gate-level wiring.




Method: This involves using a higher-level language like Verilog or VHDL to specify the multiplication algorithm. You define the steps and operations without necessarily specifying the exact gates and connections.

6- Design a hardware implementation schematic and define the number of IC chips requirements for a Binary 2-bits binary multiplier with Binary to Decimal Converter to Drive Two Seven-Segment Indicators. The Four Inputs to the Converter Circuit (A, B, C, D) as in the Figure 3. Then, examine the suitable number of the Seven segment displays.

 



Task2

1. From your exploration of the sequential logic systems, Explain the logic operation of two Master-Slave D Flip-Flop which is a sequential logic system with two stable states that can be used to store binary data. Analyze the system for logic gates, truth table, and Timing Diagram.

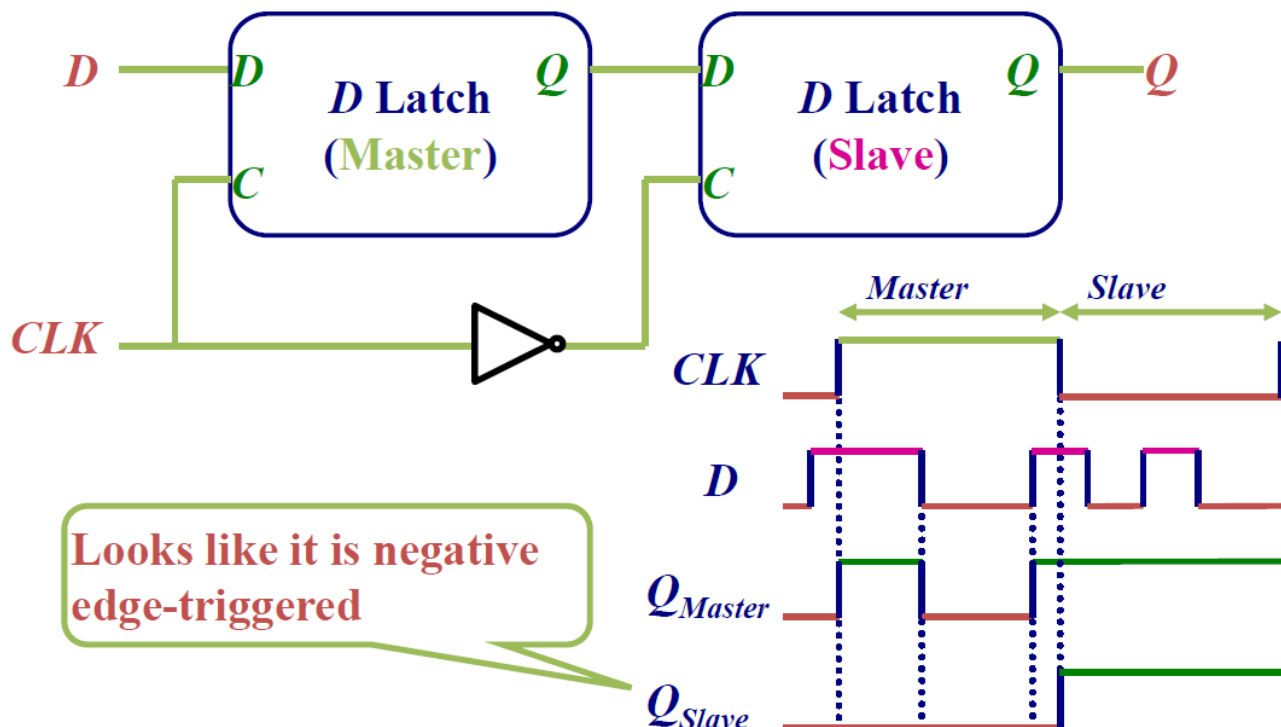 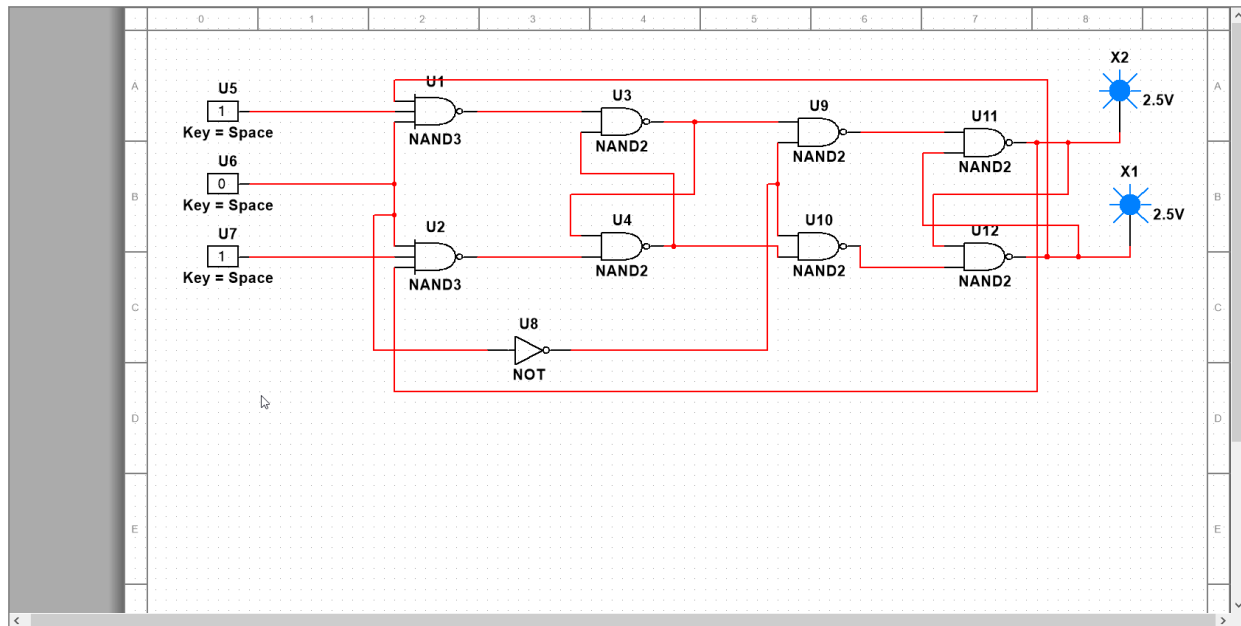

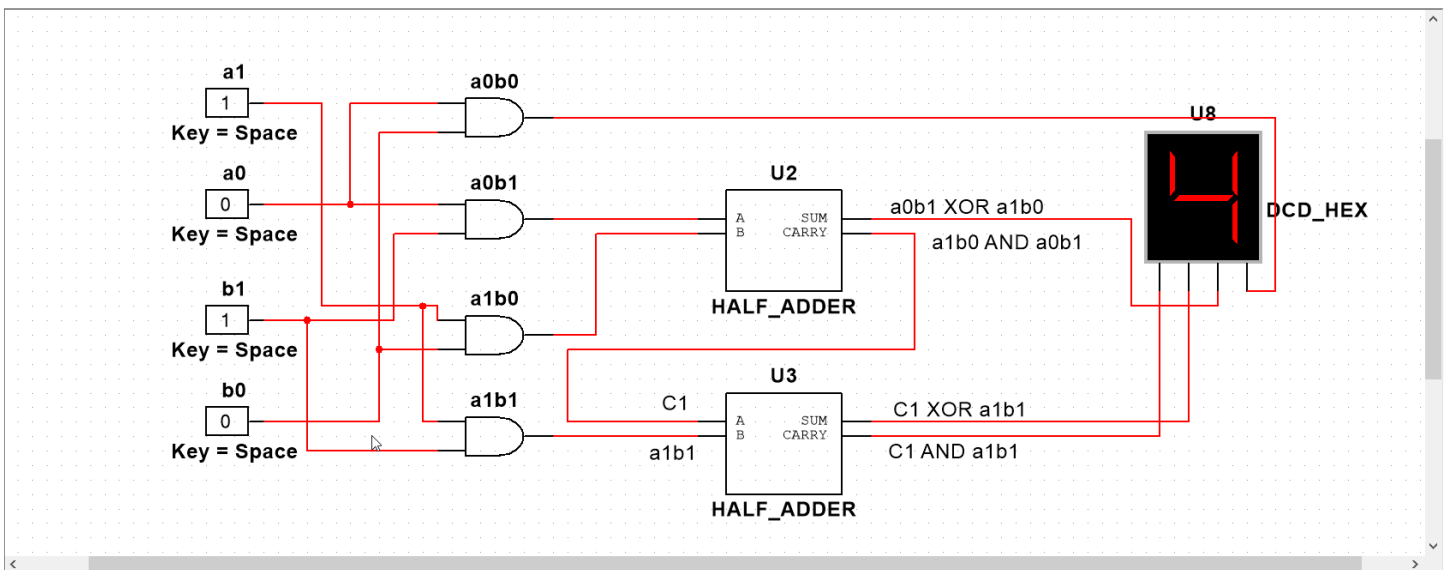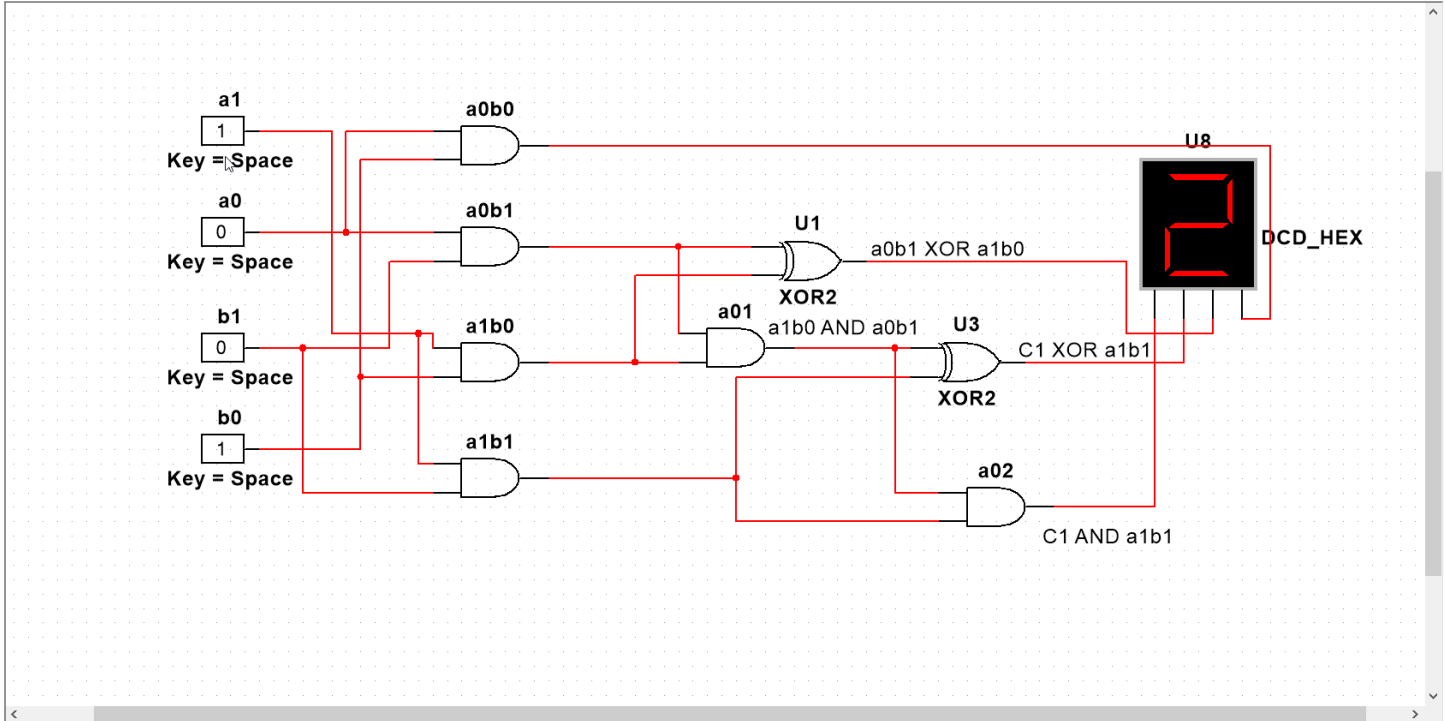Task 3

1- Use Multisim simulator to simulate the given combinational logic system and to test its operation.



Use Multisim simulator to simulate the Master-Slave D Flip-Flop and show its clock and Timing Diagram.

